



**PARISHRAM PUBLICATIONS
PUNE**

NAME of Student : _____

Subject : Physics


Class : XII

CBSE Board

Topic :- Current Electricity

Max. Marks :- 25

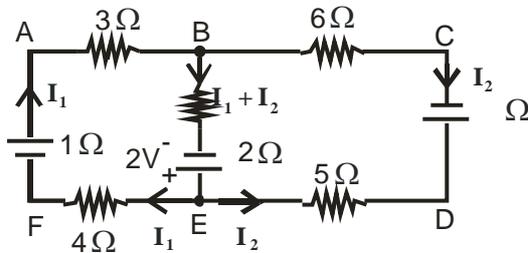1. Explain the principle of potentiometer. (2M)
2. State and explain Kirchhoff's law for electrical circuit. (3M)
3. Explain with neat circuit diagram, how will you determine the unknown resistance by using a metre bridge. (3M)
4. State any two sources of errors in metre bridge experiment. Explain how they can be minimized. (3M)
5. Find the currents through different branches and P.D. across 10Ω resistor in the network / circuit. What is the P.D. across. (4M)



6. Describe how potentiometer is used to compare the emf s of two cells lay (5M)
 - a] Direct method
 - b] combination method
7. With an unknown resistance x in the left gap and a resistance of 30Ω is the right gap of meter-bridge the will point is obtained at 40 cm from the left end of the wire. (5M)
Find : (i) the unknown resistance and
(ii) The shift in the position of the will point.
 - a] when the resistance in both the gaps are increased by 15Ω
 - b] when the resistance in each gap is sheeted by a resistance of -8Ω .